

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER– III (NEW) EXAMINATION – SUMMER 2022****Subject Code:3130305****Date:15-07-2022****Subject Name:Advanced Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

|            |  | MARKS     |
|------------|--|-----------|
| <b>Q.1</b> | (a) What do you understand by unity follower? Explain its gain term  | <b>03</b> |
|            | (b) How is an ideal an Operational Amplifier different from a Practical Operational Amplifier? Explain.  | <b>04</b> |
|            | (c) Give the internal block diagram of op-amp and mention the role of each stage.  | <b>07</b> |
| <b>Q.2</b> | (a) Draw a non-inverting amplifier using op-amp and derive expression for its output voltage.  | <b>03</b> |
|            | (b) Explain V to I converter using op-amp floating load.   | <b>04</b> |
|            | (c) What is instrumentation amplifier? Draw a circuit of instrumentation amplifier using 3 op-amps and derive the gain equation.   | <b>07</b> |
| <b>OR</b>  |  |           |
|            | (c) Draw and explain the circuit diagram of summing, scaling and averaging amplifier and write its output equation.  | <b>07</b> |
| <b>Q.3</b> | (a) Write the advantages of active filters over the passive filters.   | <b>03</b> |
|            | (b) Draw the pin diagram of AD620. Explain the features of AD620 and provide the gain equation for the same.   | <b>04</b> |
|            | (c) Draw the circuit diagram of basic integrator and practical integrator. Derive the mathematical equation.   | <b>07</b> |
| <b>OR</b>  |  |           |
| <b>Q.3</b> | (a) Define line and load regulation.   | <b>03</b> |
|            | (b) What is comparator? How op-amp can be used as comparator   | <b>04</b> |
|            | (c) Design a wein bridge oscillator using op-amp for $f_0 = 1005\text{HZ}$ .   | <b>07</b> |
| <b>Q.4</b> | (a) Draw and explain the ideal and realistic response of LP and HP filters   | <b>03</b> |
|            | (b) Explain the operation of Class A amplifier.  | <b>04</b> |
|            | (c) Draw and explain the 1st order and 2nd order active High pass filter for the cut off frequency 1.5KHz, $C = 0.01 \mu\text{f}$ . Also derive the output equation for the 1st order L.P.F. | <b>07</b> |
| <b>OR</b>  |  |           |
| <b>Q.4</b> | (a) Explain basic operation of DIAC and TRIAC.   | <b>03</b> |
|            | (b) Design a 50Hz active notch filter.   | <b>04</b> |
|            | (c) Draw and explain the circuit diagram of astable multivibrator as square wave generator.  | <b>07</b> |
| <b>Q.5</b> | (a) What do you mean by oscillator? What is the need of an oscillator?   | <b>03</b> |
|            | (b) Explain the basic structure, operation and breakover characteristics of Schockley diode.   | <b>04</b> |
|            | (c) With a neat diagram explain the comparator using an op-amp.  | <b>07</b> |

**OR**

- Q.5** (a) Explain the working principle of relay. List out the types of relays. **03**  
(b) Draw and explain the circuit diagram of Phase locked loops. **04**  
(c) Design the phase shift oscillator for  $f_0 = 200\text{Hz}$  **07**

\*\*\*\*\*