

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER– III (NEW) EXAMINATION – SUMMER 2022****Subject Code:3130306****Date:18-07-2022****Subject Name:Fundamentals of Digital Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	MARKS
Q.1 (a) Convert binary number $(10110)_2$ to Decimal, Hexadecimal and octal number.	03
(b) Subtract binary number $(101010)_2$ from $(110110)_2$ using 2's complement method.	04
(c) Draw symbol and truth table of below digital logic Gates:	07
1. AND Gate,	
2. OR Gate,	
3. NOT Gate,	
4. X-OR Gate,	
5. X-NOR Gate,	
6. NAND Gate	
7. NOR Gate.	
 Q.2 (a) Explain Gray code and covert binary number $(1111)_2$ to Gray code.	03
(b) Convert Decimal No. $(19)_{10}$ to BCD code and XS-3 code.	04
(c) Construct 4x16 decoder with two 3x8 decoders.	07
OR	
(c) Design a combinational circuit for 4 bit Magnitude Comparator.	07
 Q.3 (a) Write a brief note on Programmable Array logic (PAL).	03
(b) Realize Ex-OR gate and NOT gate using NOR gate.	04
(c) Design full subtractor using K map and realize using logic gates.	07
OR	
Q.3 (a) Write a brief note on PLA (Programmable Logic Array).	03
(b) Simplify the Boolean function using K-map: $F(w,x,y,z) = \sum m(0,1,2,4,5,6,8,9,12,13,14)$.	04
(c) Simplify the Boolean Function: $F(w,x,y,z) = \sum(1,3,7,11,15)$ and the Don't care conditions : $d(w,x,y,z) = \sum(0,2,5)$	07
 Q.4 (a) Draw symbol and truth table of D flipflop.	03
(b) Minimize the following four variable logic function using K- map: $f(A, B, C, D) = (A+B+C'+D') \cdot (A'+C+D') \cdot (A'+B+C'+D') \cdot (B'+C) \cdot (B'+C') (A+B') + (B'+D')$. Realize the circuit using logic gates.	04
(c) Draw and explain 4 bit Binary parallel adder in detail.	07
OR	
Q.4 (a) Reduce the expression:	03
1. $A+AB+ABC+ABCD$	
2. $A+A'BC+ABD+1$	
3. $A+A'B$	
(b) Explain the operation of master slave J-K flip flop.	04

(c) Simplify the Boolean function using the tabulation method **07**
 $F(A,B,C,D,E,F,G)=\Sigma(20,28,38,39,52,60,102,103,127)$.

Q.5 (a) Convert SR flip-flop into T flip-flop. **03**

(b) Write a short note on shift register. **04**

(c) Design circuit for 4-bit ring counter. **07**

OR

Q.5 (a) Explain 2 bit binary UP counter using JK flip-flops **03**

(b) Explain the working of 4-bit Johnson counter. Write the count sequence obtained at the output. **04**

(c) Explain with logic diagram of 4-bit serial-in serial-out shift register. **07**
