

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III(NEW) EXAMINATION – SUMMER 2023****Subject Code:3130305****Date:28-07-2023****Subject Name:Advanced Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Why Op-Amp is called versatile device? Give pin diagram of Op-Amp.	03
	(b) Explain Open loop Inverting and Non-inverting amplifier.	04
	(c) Design instrumentation amplifier with the gain of 10.	07
Q.2	(a) Enlist ideal characteristics of Op-Amp.	03
	(b) Compare Inverting and Non-inverting amplifier.	04
	(c) Explain how Op-Amp can work like Summing, Scaling and averaging amplifier.	07
OR		
	(c) Explain the circuit of Op-amp as Differentiator. Also derive equation of gain.	07
Q.3	(a) Design an amplifier for gain 03. Also draw sample input-output waveforms.	03
	(b) Justify following characteristic of Ideal Op-Amp: The output impedance (R_o) must be zero.	04
	(c) Explain the design of 1 st order High pass op-amp filter.	07
OR		
Q.3	(a) For the below given circuit, calculate Output voltage V_o . Consider input DC voltage $V_1=3$ Volt & $V_2=5$ Volt.	03
	(b) Justify following characteristic of Ideal Op-Amp: The input impedance (R_i) must be infinite.	04
	(c) Explain the design of band stop op-amp filter.	07
Q.4	(a) Explain working principle of Electromagnetic relay.	03

- (b) Design Phase-shift oscillator for oscillation frequency 200 Hz. **04**
(c) Explain structure and operation of SCR. **07**
- OR**
- Q.4** (a) Explain working principle of solid state relay. **03**
(b) Enlist application of 555 Timer. Explain working of astable operation. **04**
(c) Explain basic construction and operation of UJT. **07**
- Q.5** (a) Write brief note on any two types of Op-Amp noise. **03**
(b) Explain the working of Phase locked loop circuit. **04**
(c) Explain Operation of Class B amplifier. **07**
- OR**
- Q.5** (a) Explain basic operation of DIAC & TRIAC. **03**
(b) Explain working of transistor as a switch. **04**
(c) Explain functioning of differential amplifier using transistors. **07**
