

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE- SEMESTER-III (NEW) EXAMINATION – WINTER 2020****Subject Code:3130704****Date:05/03/2021****Subject Name:Digital Fundamentals****Time:10:30 AM TO 12:30 PM****Total Marks:56****Instructions:**

1. Attempt any FOUR questions out of EIGHT questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

	MARKS
<b>Q.1</b> (a) Realize AND, OR and NOT gate using NAND gates only.	<b>03</b>
(b) State and prove De-Morgan's theorems using truth-tables.	<b>04</b>
(c) Do as directed:	<b>07</b>
(a) $(1111.11)_2 = (? )_8 = (? )_{10}$	
(b) $23 - 48$ using 2's complement method	
(c) $(396)_{10} = (? )_{BCD} = (? )_{EX-3}$	
(d) $(11111)_2 = (? )_{Gray}$	
<b>Q.2</b> (a) Define following: Figure of merit, Noise margin, and Power dissipation.	<b>03</b>
(b) Construct Hamming code for BCD 0110. Use even parity.	<b>04</b>
(c) Given a logic function: $Z = ABC + BC'D + A'BC$ .	<b>07</b>
(i) Make a truth table.	
(ii) Simplify using K-map.	
(iii) Realize simplified function using NAND gates only.	
<b>Q.3</b> (a) Draw the logic diagram of 1-digit BCD adder.	<b>03</b>
(b) Minimize following Boolean function using K-map:	<b>04</b>
$Y(A,B,C,D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$	
(c) Write a brief note on race around condition and its solution. Draw & explain the logic diagram of master-slave JK flip-flop.	<b>07</b>
<b>Q.4</b> (a) Draw truth table of 2-bit digital comparator.	<b>03</b>
(b) Minimize following Boolean function using K-map:	<b>04</b>
$F(A,B,C,D) = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$	
(c) Design a 4-bit synchronous down counter using T flip-flops.	<b>07</b>
<b>Q.5</b> (a) Design D FF using SR FF. Write truth table of D FF.	<b>03</b>
(b) Draw & explain in brief the logic diagram of 4-bit bidirectional shift register.	<b>04</b>
(c) List out various commonly used D/A converters. Draw & explain any one D/A converter.	<b>07</b>
<b>Q.6</b> (a) List out and explain any one application of the register.	<b>03</b>
(b) Design a 4-bit ripple up counter using JK flip-flops.	<b>04</b>
(c) List out various commonly used A/D converters. Draw & explain any one A/D converter.	<b>07</b>
<b>Q.7</b> (a) Draw internal organization of a 16 x 4 memory chip.	<b>03</b>
(b) Write a brief note on quantization and encoding.	<b>04</b>
(c) Write a detailed note on various types of memories.	<b>07</b>

- Q.8** (a) List out various characteristics of a D/A converter. Discuss any one. **03**  
(b) Obtain 2048 x 8 memory using 256 x 8 memory chips. **04**  
(c) Draw and explain in detail the block diagram of CPLD. **07**

\*\*\*\*\*