

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (NEW) EXAMINATION – WINTER 2021****Subject Code:3130907****Date:21-02-2022****Subject Name:Analog & Digital Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	MARKS
Q.1 (a) Define following a) CMRR b)PSRR c)Input Offset voltage	03
(b) What is cross over distortion in power amplifier?	04
(c) Draw and explain the equivalent circuit of OP-Amp.	07
Q.2 (a) Define Slew Rate .Also mention about causes of slew rate.	03
(b) Draw the basic Integrator using OP-Amp. Derive the output equation of Integrator.	04
(c) Derive an expression for the output of a Inverting Summing amplifier with three input and Average amplifier.	07
OR	
(c) Discuss the classification of active filter and explain the frequency response of each type.	07
Q.3 (a) Simplify $\bar{A}BC\bar{D} + BC\bar{D} + B\bar{C}\bar{D} + B\bar{C}D$	03
(b) Realize expression using minimum NAND gates only $Y = A\bar{B} + A\bar{C} + C + AD + A\bar{B}C + ABC$	04
(c) For the following function implement the SOP and POS circuit $F(A,B,C,D) = \sum m (2,3,5,7,12) + \sum d (6,13,14,15)$	07
OR	
Q.3 (a) Simplify the Boolean function with K map $F(a, b, c, d) = \sum (0,1,2,4,5,6,8,9,12,13,14)$	03
(b) Implement the following function using 8:1 Multiplexer. $F(A,B,C,D) = \bar{A}B\bar{D} + ACD + \bar{B}CD + A\bar{C}D$	04
(c) Explain Half Adder circuit .Explain Full adder circuit with the help of two Half adder.	07
Q.4 (a) Compare RC phase shift and Wien bridge oscillator.	03
(b) Write a short note on Precision rectifier.	04
(c) Explain the working of Zero crossing Detector.	07
OR	
Q.4 (a) Define following a) Attenuation b) Pass Band c) Cut of frequency	03
(b) Draw the peak detector circuit using Op-amp and explain it's operation.	04
(c) Draw and explain the block diagram of basic three terminal IC Regulator.	07
Q.5 (a) Explain the different types of triggering methods used for flip flops.	03
(b) Write a note on serial in parallel out operation of shift register.	04
(c) Explain the Binary Weighted register technique of D/A converter.	07

OR

- Q.5** (a) Define following specification of DAC **03**
a) Accuracy b) Resolution c) Setting time
- (b) Which are the different methods for A/D conversion ? **04**
- (c) Draw and explain the working of 4 bit Ring counter. **07**
