

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (NEW) EXAMINATION – WINTER 2021****Subject Code:3130305****Date:21-02-2022****Subject Name:Advanced Electronics****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Explain the working principle of the relay with the help of a diagram.	03
	(b) Draw and explain a block diagram of an operational amplifier.	04
	(c) Draw and explain differential amplifier using transistor.	07
Q.2	(a) List out the ideal characteristics of Op-amp.	03
	(b) Explain the importance of Virtual ground with a help diagram.	04
	(c) Draw and explain a closed-loop configuration of Inverting and Non inverting amplifier. Derive the gain equation.	07
OR		
	(c) Draw and explain the Op-amp based differential amplifier and derive the gain equation.	07
Q.3	(a) List out the application of the Instrumentation amplifier and mention essential characteristics.	03
	(b) Draw a circuit diagram of voltage follower and derive the gain equation.	04
	(c) Draw and explain the integrator circuit and derive its equation.	07
OR		
Q.3	(a) List out different Noise sources, and its effect on output response.	03
	(b) Draw an ideal response of Filters.	04
	(c) Write a brief note on Noise Colors.	07
Q.4	(a) Draw a Guard driving with AD620.	03
	(b) Design a 2 nd Order Low Pass filter. (Cut of Frequency – 500 Hz)	04
	(c) Design an active notch filter of 50 Hz.	07
OR		
Q.4	(a) Define Oscillator. List out the different types of Oscillators.	03
	(b) Draw and explain the operation of the Class A amplifier in detail.	04
	(c) Explain the load and line regulation in detail.	07
Q.5	(a) Draw and explain V to I converter circuit	03
	(b) Explain the essential operation of DIAC.	04
	(c) Design the wein bridge oscillator using op-amp for $f_0 = 500$ Hz.	07
OR		
Q.5	(a) List out the application of Power Amplifier and mention their types.	03
	(b) Draw and explain the 1st and 2nd order active High pass filter for the cut off frequency 1 KHz, $C = 0.1\mu\text{f}$.	04
	(c) Draw and explain the circuit diagram of an astable multivibrator as a square wave generator.	07
