

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (NEW) EXAMINATION – WINTER 2021****Subject Code:3130704****Date:23-02-2022****Subject Name:Digital Fundamentals****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

MARKS

- Q.1** (a) Implement EX-NOR using NAND gate. **03**
 (b) Convert the decimal number 225.225 to octal and hexadecimal. **04**
 (c) Give classification of logic families and compare CMOS and TTL. **07**
- Q.2** (a) Convert $F(A,B,C) = BC+A$ into standard minterm form. **03**
 (b) With logic diagram and truth table, explain the working of 3 line to 8 line decoder. **04**
 (c) Explain Successive Approximation A/D converter in detail. **07**
- OR**
- (c) A combinational logic is defined by functions: **07**
 $F_1(A,B,C) = \sum m(3,5,6,7)$ $F_2(A,B,C) = \sum m(0,2,4,7)$
 Implement the circuit with PLA having 3 inputs, 4 product terms & 2 outputs.
- Q.3** (a) Simplify the Boolean expression: $F(x,y,z) = \sum m(0,1,3,4,5,7)$ **03**
 (b) Explain S-R clocked flip flop. **04**
 (c) Design full adder circuit using decoder and multiplexer. **07**
- OR**
- Q.3** (a) Generate AND & EX-OR gates using NOR gate. **03**
 (b) Implement D flip flop using JK flip flop. **04**
 (c) Design a counter to generate the repetitive sequence 0,4,2,1,6. **07**
- Q.4** (a) What is race around condition in JK flip flop. **03**
 (b) Construct a ring counter with five timing signals. **04**
 (c) Design BCD to Excess 3 code converter using minimum number of NAND gates. **07**
- OR**
- Q.4** (a) Explain 2-bit comparator circuit. **03**
 (b) Write a short note on FPGA. **04**
 (c) What is Digital to Analog converter? Draw and Explain R-2R DAC. **07**
- Q.5** (a) Perform following operation using 2's complement method. **03**
 $(11010)_2 - (1000)_2$
 (b) Write a short note on Read Only Memory (ROM). **04**
 (c) Explain the working of 4 bit binary ripple counter. **07**
- OR**
- Q.5** (a) Obtain the truth table of the function: $F = xy+yz+zx$. **03**
 (b) Implement following functions using ROM. **04**
 $F_1 = \sum m(1,3,4,6)$ and $F_2 = \sum m(0,1,5,7)$.
 (c) Explain in detail Dual Slope A/D converter. **07**
