

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III (NEW) EXAMINATION – WINTER 2021****Subject Code:3131102****Date:21-02-2022****Subject Name:Digital System Design****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

Q.1 (a) Draw the logic circuit for the following Boolean function using NAND gates only. **03**

$$F(x, y, z) = xy + yz + xz$$

(b) State the De-Morgan's Law and find the complement of the following Boolean function in Product-of-Sum (POS) form using De-Morgan's Law. **04**

$$F(A, B, C, D) = AB'(C+D) + C'D(A'+B)$$

(c) Simplify the following Boolean function using **Karnaugh Map (K-map)** method. **07**

$$F(A, B, C, D) = (A' + B' + D')(A + B' + C')(A' + B + D')(B + C' + D')$$

Realize the simplified function using **NOR Gates** only.

Q.2 (a) State the duality theorem. Also find the dual of the following Boolean expression. **03**

$$(x + y)(x' + z)(y + z) = (x + y)(x' + z)$$

(b) Simplify the following Boolean expression using Boolean Algebra. **04**

$$(i) x' + xy + xz' + xy'z'$$

$$(ii) A'B(D' + C'D) + B(A + A'CD)$$

(c) Explain the working of Master-Slave SR Flip-flop with Logic diagram and waveforms. **07**

OR

(c) Draw the logic circuit of **4-to-1 Multiplexer** and explain its working with the help of truth-table. **07**

Q.3 (a) Draw truth-table and logic circuit for **2-bit magnitude comparator**. **03**

(b) Explain the following parameters for Digital Integrated Circuits. **04**

(i) Fan-out

(ii) Fan-in

(iii) Propagation Delay

(iv) Noise Margin

(c) Find the prime implicants for the following Boolean function by means of the Tabulation Method. **07**

$$F(A, B, C, D, E) = \Sigma m(2, 3, 8, 9, 12, 13, 18, 19, 25, 27, 29, 31)$$

OR

Q.3 (a) Explain working of **4-bit Binary Adder circuit** with the neat logic diagram. **03**

(b) Compare TTL and CMOS logic families. **04**

(c) Simplify the following Boolean function **F** together with the don't-care conditions **d** in sum-of-products (SOP) using **Karnaugh Map (K-map)** method. **07**

$$F(A, B, C, D) = \Sigma m(3, 4, 13, 15) \text{ and } d(A, B, C, D) = \Sigma m(1, 2, 5, 6, 8, 10, 12, 14)$$

- Q.4** (a) State the difference between asynchronous and synchronous sequential logic circuits with suitable example. **03**
- (b) What is State Machine? Explain the need of State Machine in Digital Systems. **04**
- (c) A sequential circuit with two D flip-flops (*A and B*); one input (*x*); and one output (*y*) is specified by the following state table: **07**

<i>Present State</i> (<i>AB</i>)	<i>Next State (AB)</i>		<i>Output (y)</i>	
	<i>x = 0</i>	<i>x = 1</i>	<i>x = 0</i>	<i>x = 1</i>
00	01	00	1	0
01	01	11	0	1
10	00	10	0	1
11	11	10	1	0

Derive the next-state equations, output equation and draw the state diagram.

OR

- Q.4** (a) State and explain different types of triggering for Flip-flops. **03**
- (b) State the different types of Shift-Registers and explain working of the Serial-In Serial-Out shift register with neat diagram. **04**
- (c) Design modulo-10 ripple up counter and explain its working using neat logic diagram and waveforms. **07**

- Q.5** (a) Define: Register, Ripple counter, Synchronous counter. **03**
- (b) State various types of **Digital-to-Analog converters** and briefly explain working principle of any. **04**
- (c) Draw and explain PLA block diagram. Also draw the Programmable Logic Array with three inputs, three product terms, and two outputs. **07**

OR

- Q.5** (a) Briefly explain the steps for VLSI design flow. **03**
- (b) Realize T Flip-flop functionality using D Flip-flop only. **04**
- (c) Explain dual slope type **Analog-to-Digital converter** in detail with neat diagram. **07**
