

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER- III(NEW) EXAMINATION – WINTER 2022****Subject Code:3130305****Date:24-02-2023****Subject Name:Advanced Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

	MARKS
Q.1 (a) What is Transistor?	03
(b) Explain operation of Transistor in CB configuration.	04
(c) Design a power supply with +9V & -9V output by specifying all component names and values.	07
Q.2 (a) Draw & explain pin diagram of 741 op-amp.	03
(b) Explain ideal characteristics of op-amp.	04
(c) Enlist the types of Relays and explain any one with neat diagram.	07
OR	
(c) Design Instrumentation amplifier of 1000 gain using 3 op-amps.	07
Q.3 (a) Describe Voltage follower with its need.	03
(b) Design op-amp based Integrator circuit with input-output waveforms.	04
(c) Explain different close loop configuration of op-amp with output voltage equation.	07
OR	
Q.3 (a) Describe various Noise sources in op-amp.	03
(b) Design op-amp based Differentiator circuit with input-output waveforms.	04
(c) Explain application of op-amp as summing, scaling and averaging amplifier with equations.	07
Q.4 (a) Explain different oscillator principles.	03
(b) Draw approximate response of different types of filters.	04
(c) Design 120 Hz 2 nd order Butterworth low-pass filter. (C=1 μ F)	07
OR	
Q.4 (a) Write a short note on Wein bridge oscillator.	03
(b) Explain 555 Timer circuit as Astable multivibrator.	04
(c) Design 50 Hz active Notch filter. (C=0.1 μ F)	07
Q.5 (a) Enlist types of Power amplifier with its operating region.	03
(b) Draw VI characteristics & symbol for DIAC and TRIAC.	04
(c) Explain basic structure and operation of Schockley Diode.	07
OR	
Q.5 (a) Describe Class-AB push pull operation of amplifier.	03
(b) Explain the Operation of Class-A power amplifier.	04
(c) Explain basic structure and operation of SCR.	07
