

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER- III(NEW) EXAMINATION – WINTER 2022****Subject Code:3130306****Date:27-02-2023****Subject Name:Fundamentals of Digital Electronics****Time:02:30 PM TO 05:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

		MARKS
Q.1	(a) Subtract the following Binary numbers using 1's complement method, 111000101-101101	03
	(b) Explain Universal Gates with truth table.	04
	(c) Explain Full Adder with truth table and Logic Diagram.	07
Q.2	(a) Encode data bits 1010 into the 7-bit even parity Hamming code.	03
	(b) Prove De Morgan theorem with truth table.	04
	(c) Explain Full Subtractor with truth table and Logic Diagram.	07
	OR	
	(c) Design 3-bit Magnitude Comparator.	07
Q.3	(a) Draw logic diagram of Boolean expression $f = A + \overline{ABD} + \overline{ABC} + \overline{ABCD}$.	03
	(b) Expand $f = C(A+B)$ to maxterms and minterms.	04
	(c) Design 16:1 MUX using 4:1 MUX (Multiplexer) Modules.	07
	OR	
Q.3	(a) Explain Octal to Binary Encoder.	03
	(b) Explain 3-Line to 8-Line Decoder with logic Diagram.	04
	(c) Find the minimal expression for $f = \sum m\{2,3,4,7,11,12,13\}$ using Kmap.	07
Q.4	(a) Explain D Flip –flop.	03
	(b) Reduce the Boolean Expression $f = \sum m\{0, 2,3,4,7\}$ using tabular Method.	04
	(c) Design 4-bit Gray to Binary Code Converter.	07
	OR	
Q.4	(a) Implement Half adder with Programmable Logic Array.	03
	(b) Explain Serial IN, Serial Out shift register.	04
	(c) Explain Positive Edge triggered S-R and J-K Flip Flops.	07
Q.5	(a) Write Excitation Tables of J-K Flip Flop and T-Flip Flop.	03
	(b) Explain Master- Slave J-K flip flop.	04
	(c) Design Asynchronous Two-bit Ripple UP-Counter using Negative Edge-triggered J-K Flip-Flops.	07
	OR	
Q.5	(a) Explain Applications of Flip Flops.	03
	(b) Describe Conversion of J-K flip flop to T flip flop.	04
	(c) Design Synchronous 3-bit UP Counter using JK flip flop.	07
